

# P-N-P-N Switching Device

①

Electronic device  $\rightarrow$  Switching is very important (most common application)  
 $\Downarrow$

Device change an 'off' or blocking state to 'on' or conducting state.

Switching device :-

- ① Transistor  $\rightarrow$  Base current drives the device from cut-off to saturation.

- ② Diodes

Device; Remain blocking state under forward bias  
Switched to  $\Downarrow$  Triggered by an external signal.  
Conducting state.

---

SCR  $\Rightarrow$  Semiconductor Controlled rectifier  
or

Silicon controlled rectifier (As Si is the common material used)

under forward bias :-


High impedance is 'off' condition  
(until a switching signal applied)

After switching  $\rightarrow$  Low impedance (ON condition)

Signal  $\rightarrow$  (for switching)  $\rightarrow$  may be apply or vary externally.

These device  $\rightarrow$  Block/Pass current at predetermined levels.

# Basic Structure

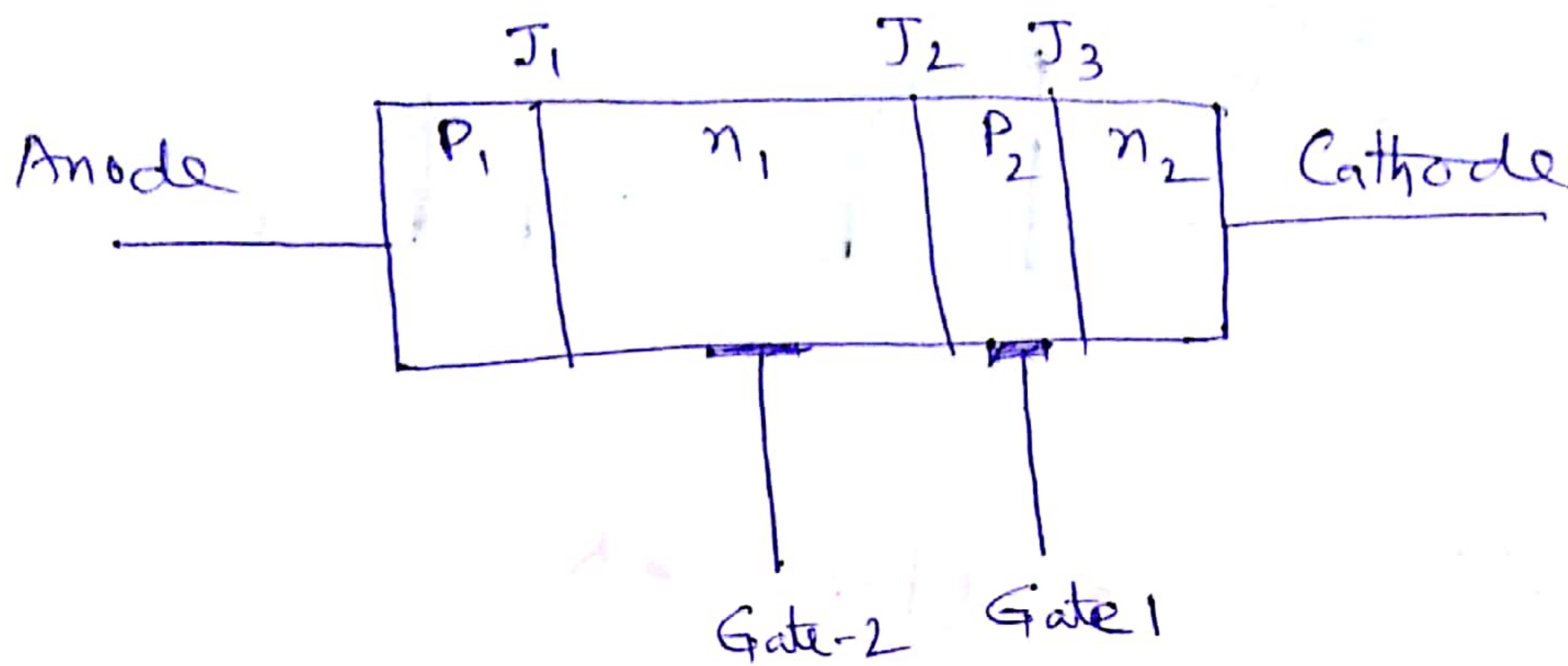

4-layer p-n-p-n device.


3 - p-n junctions  $J_1$ ,  $J_2$  and  $J_3$  in series.

Contact electrodes.


- ① Anode  $\rightarrow$  electrode attached outer p-layer
- ② Cathode  $\rightarrow$  " " " n-layer
- ③ base  $\rightarrow$  Two gate electrodes (Gate-1 & Gate-2)

without gate electrode! - The device is operated as a two terminal p-n-p-n or sh. diode or Shockley diode.

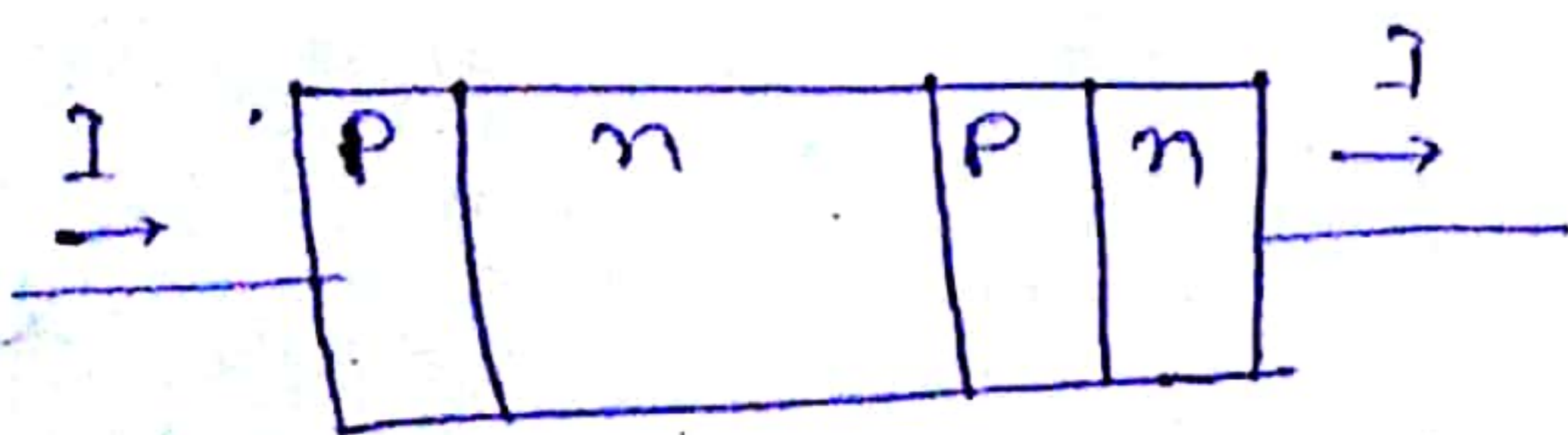with one gate electrode! - Three terminals device, called SCR or thyristor.



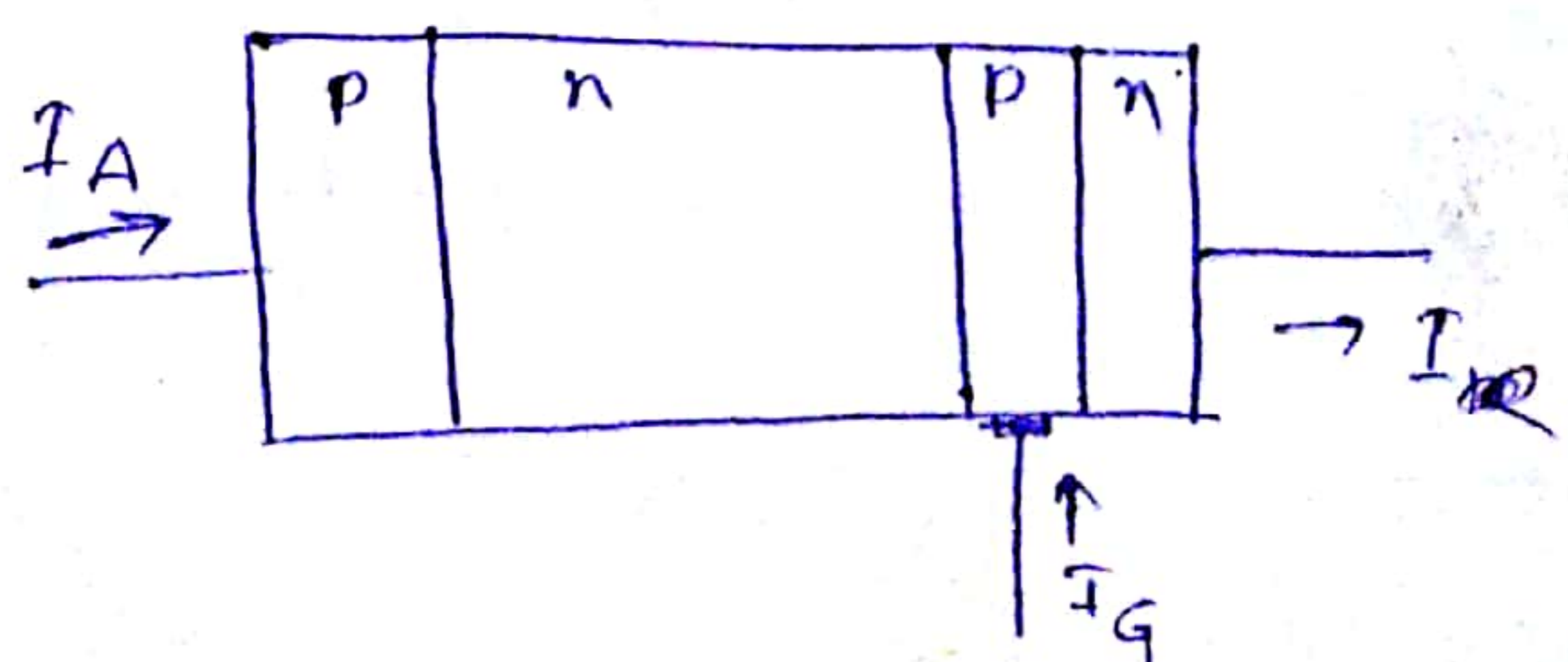
2-terminal p-n-p-n-diode  
or  
Shockley diode



3-terminal thyristor

## Doping profile

Impurity density ↑

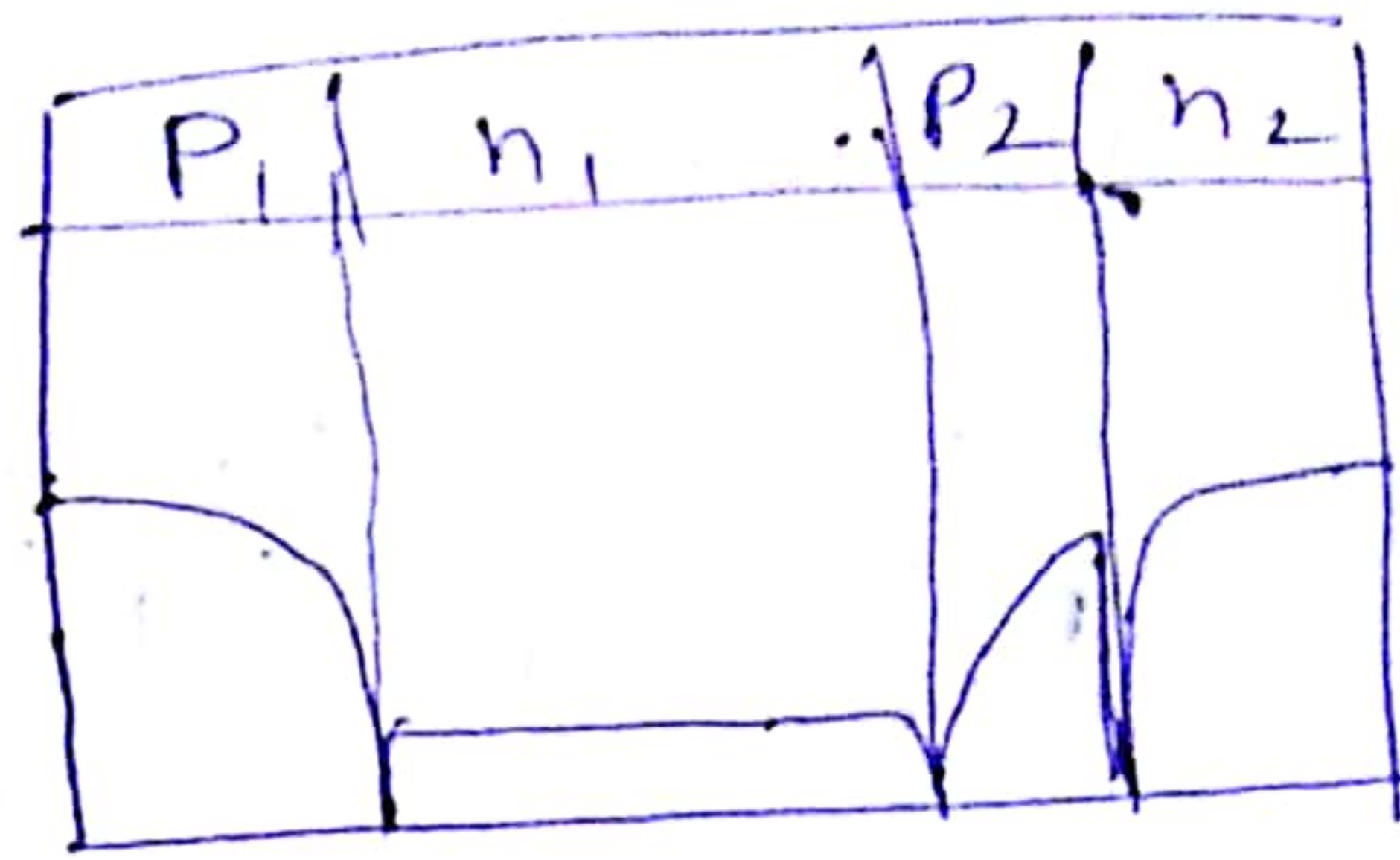


## Common-circuit symbol:



## Forward bias:

Anode is ~~po~~ +vely biased w.r.t. Cathode.

Anode → +ve  
Cathode → -ve.

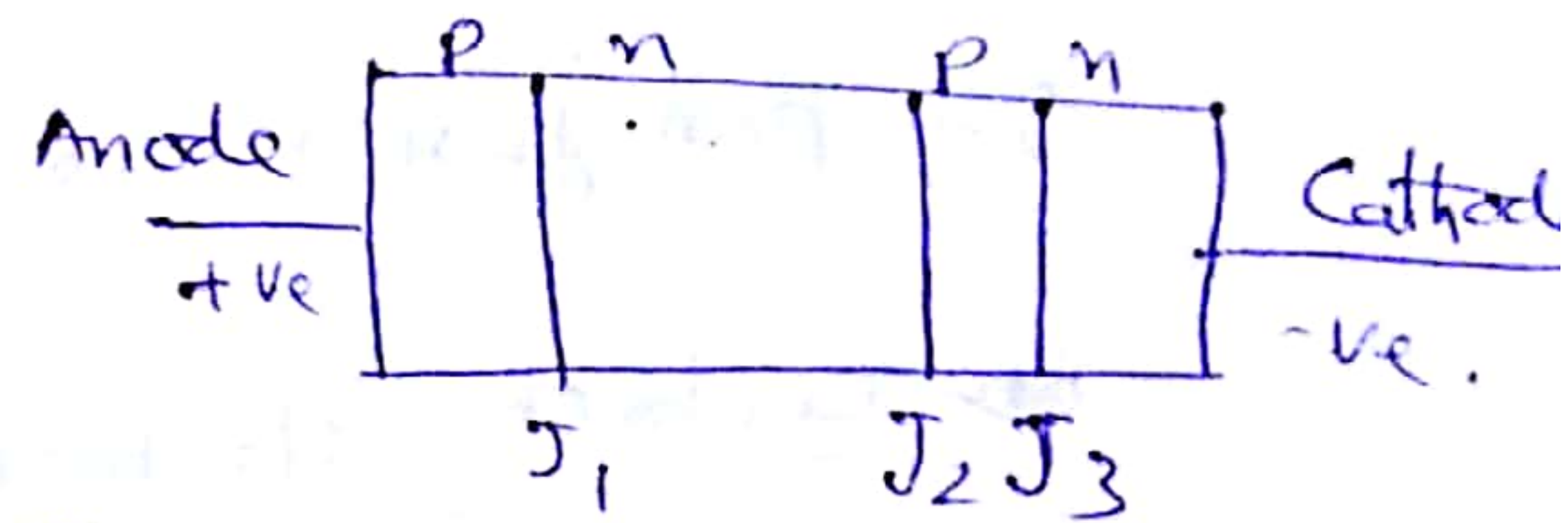


Here → junction  $J_1$  &  $J_3$  → Forward bias  
 $J_2$  → Reverse bias

## Reverse bias:

Anode is -ve w.r.t. Cathode.


Anode → -ve  
Cathode → +ve

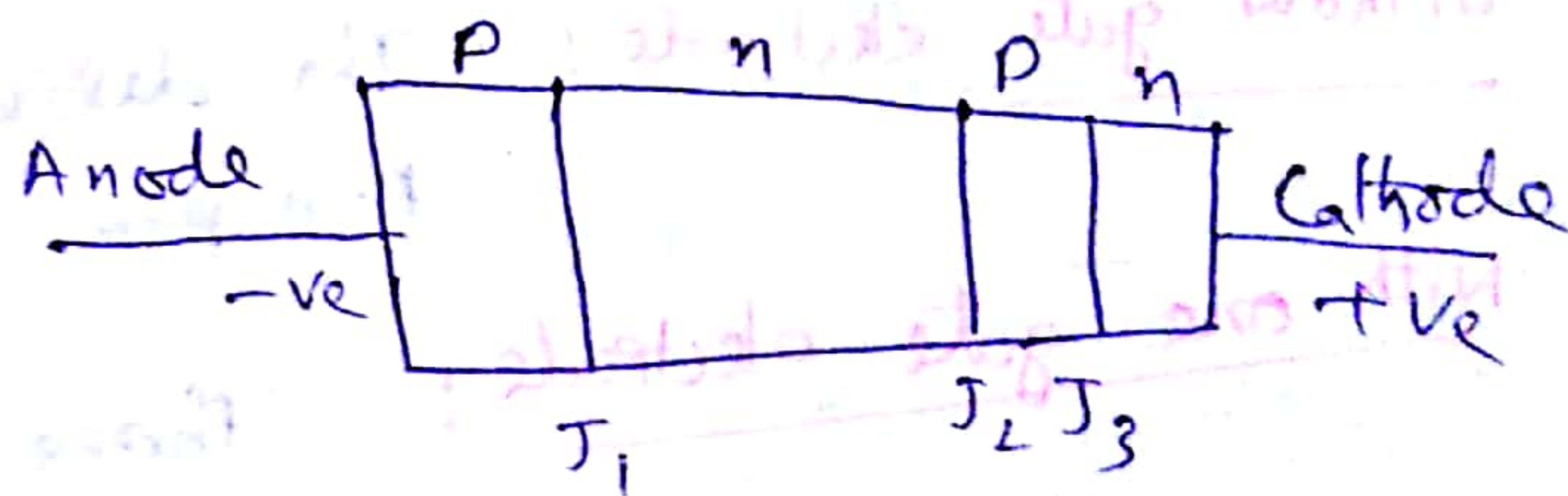

$J_1$  &  $J_3$  → Junction → Reverse bias

$J_2$  → forward bias.

V - Characteristics :-

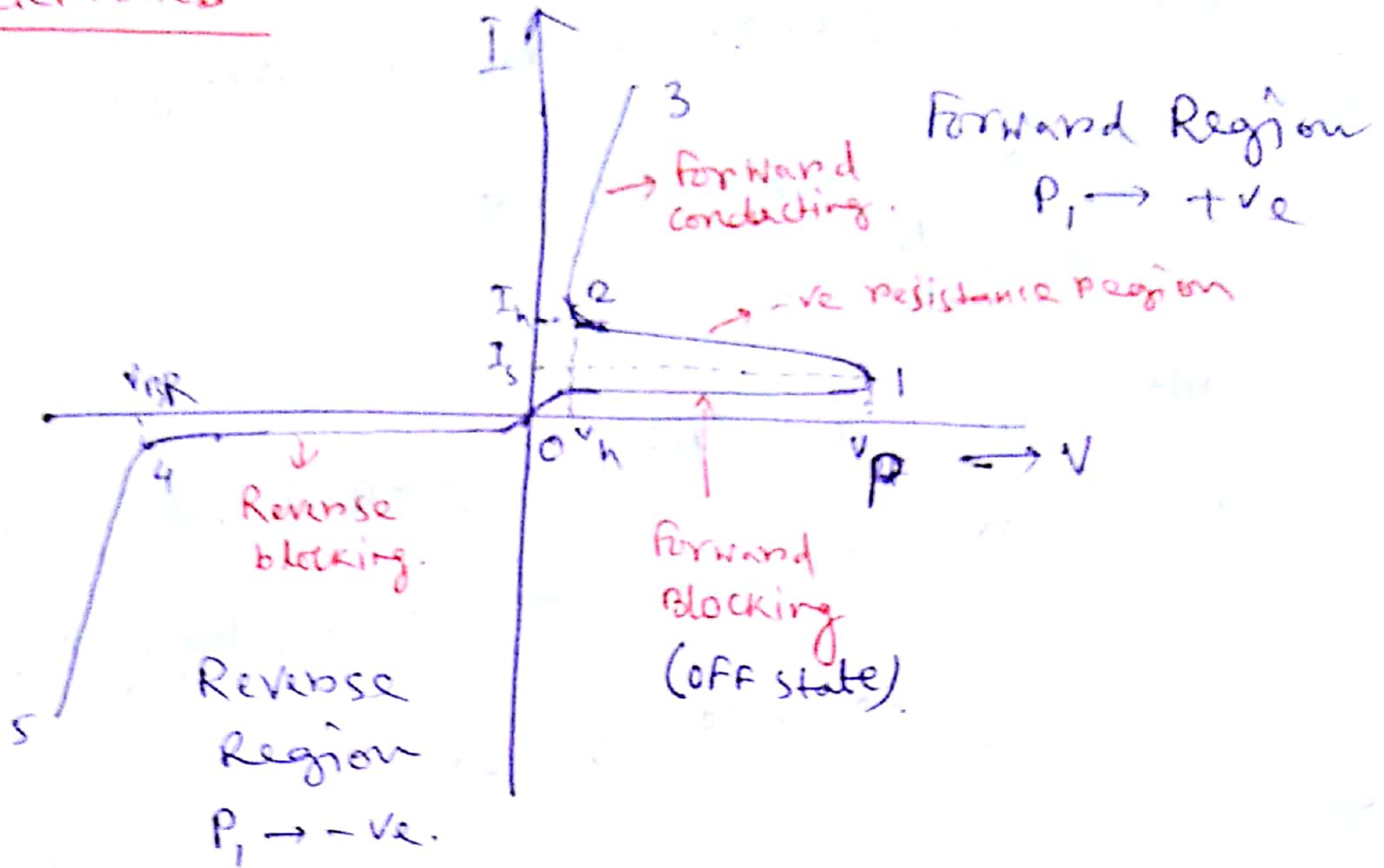

Region

0 → 1 ⇒ Forward blocking or OFF state  
very High impedance state

at 1 → forward Breakover or switching occurs  
Here  $\frac{dV}{dI} = 0$  at  $V_p$

$V_p$  ⇒ Device switches from blocking to conducting state.  
called → critical peak forward voltage  
or forward breakover voltage.

$I_s$  → switching current or turn-on current.  
1 → 2 ⇒ -ve resistance region

2 → 3 ⇒ Forward conducting or ON state.

At point 2 ⇒  $\frac{dV}{dI} = 0$ ,  $I_h$  → holding current  
 $V_h$  → holding voltage.

Reverse Region

0 - 4 ⇒ Reverse blocking state

4 → 5 ⇒ Reverse breakdown region.

\*\*\*

Thyristor  $\rightarrow$  operated in forward region.

$\Downarrow$   
a Bi-stable device  
cause  $\Downarrow$   
 $\Downarrow$

Switch from  $\Rightarrow$  High impedance, low current OFF state  
Switch to  $\Rightarrow$  low impedance, high current ON state  
OR vice versa.

---

In forward blocking state: when voltage increase,  $\rightarrow$  most of forward voltage  $\rightarrow$  appears across the reverse-biased junction  $J_2$ .

In Forward - conducting state: All 3-junctions must be forward bias.




In Reverse - blocking state: - supply of electron & holes to  $J_2$  is restricted by the reverse-biased junction on either side.  
current is limited to  $\rightarrow$  small saturation current arising from thermal generation of EHP.

Reverse breakdown  $\rightarrow$  Breakdown (avalanche) occurs.

---

At forward break down voltage  $\rightarrow$  The current reaches  $I_S$ ,  
 $\rightarrow$  break down occurs  $\rightarrow$  characteristic curve traversed rapidly (within  $\mu s$ ) to reach  $I_H$ .

# Twe-Transistor Analogy

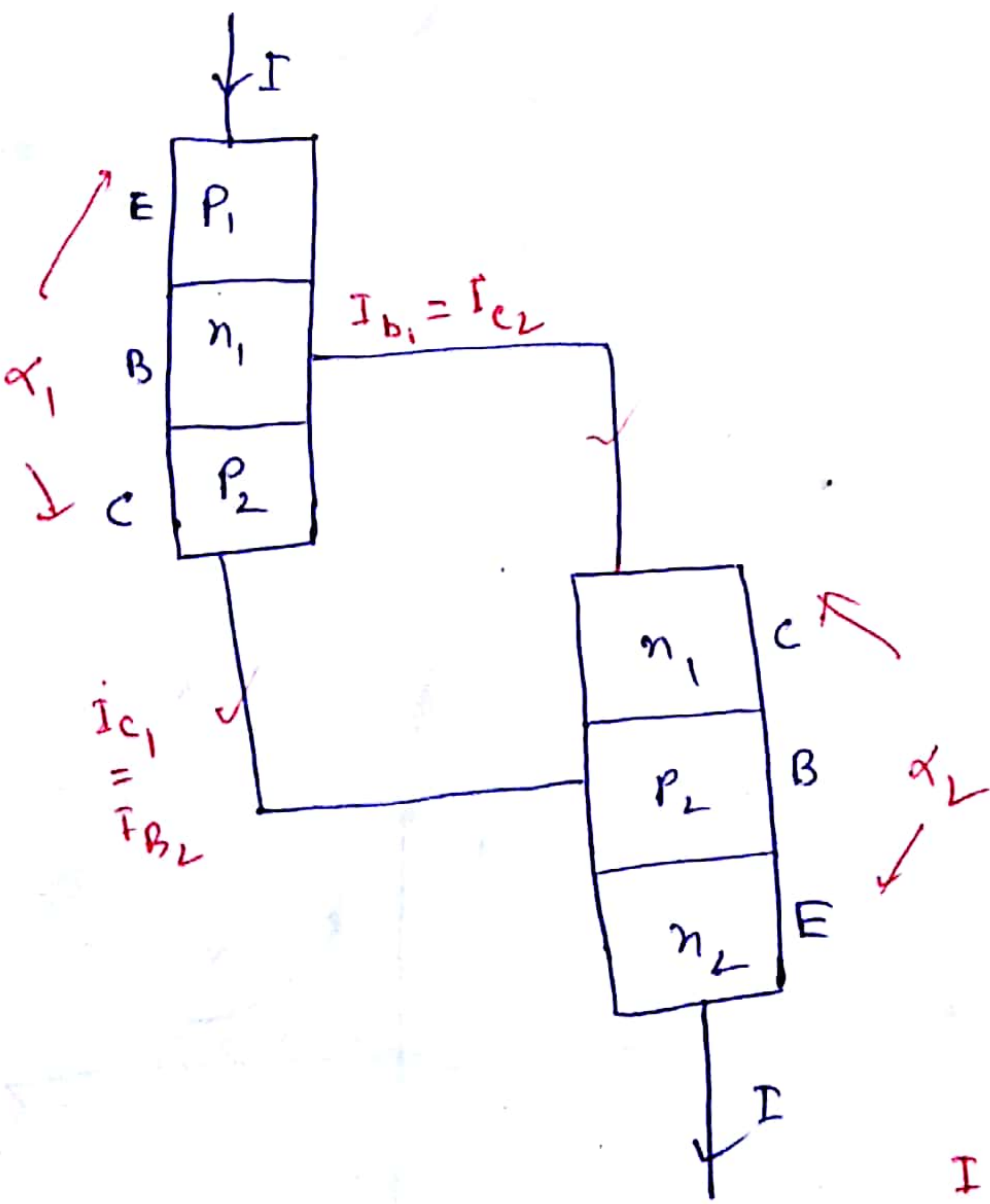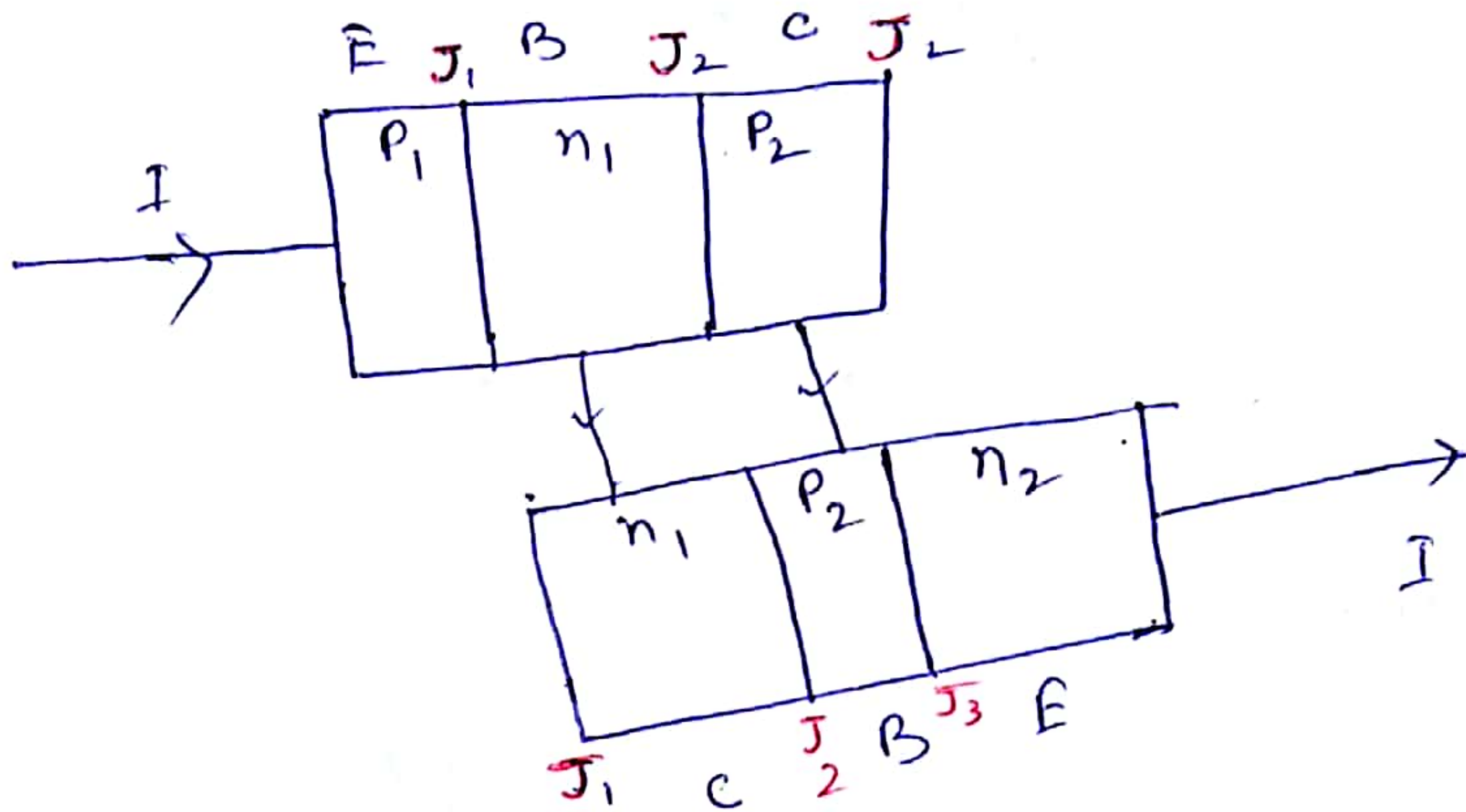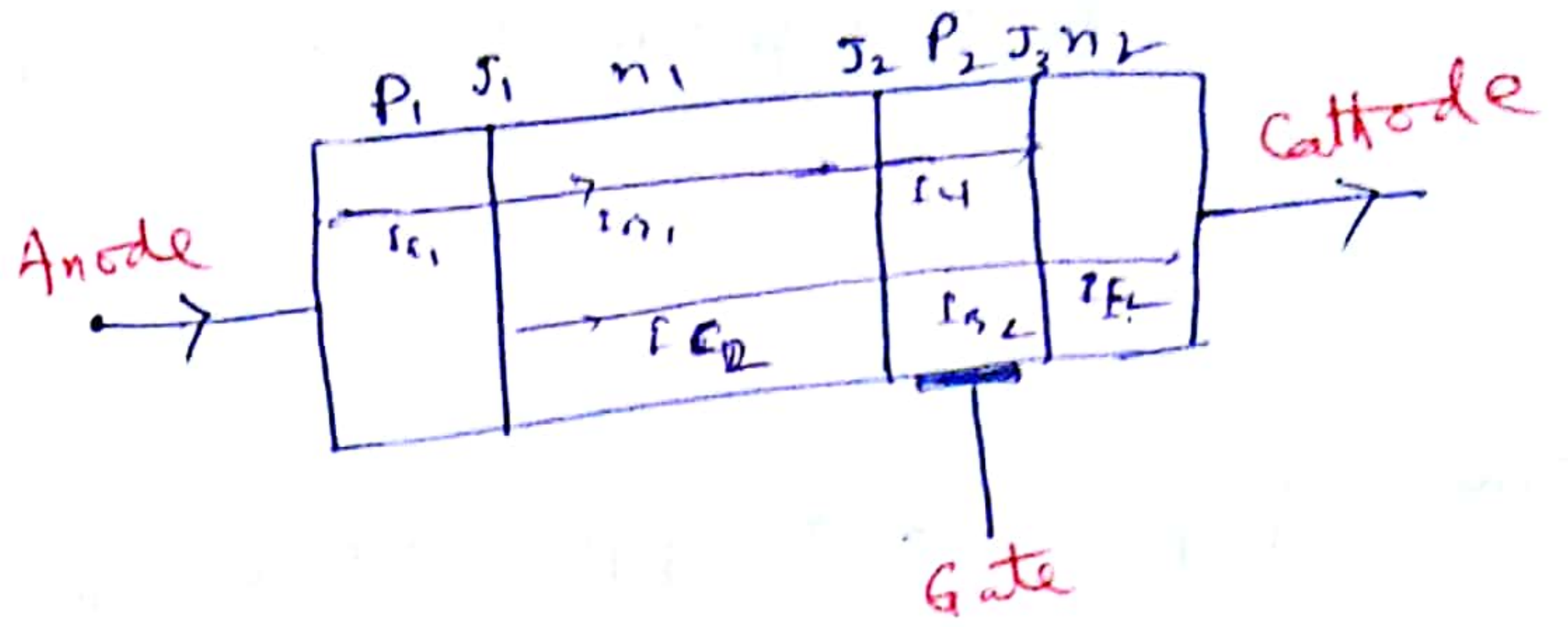

$I_{C0}$  → Reverse saturation current

$$I_{C1} = \alpha_1 I + I_{C01} = I_{B2}$$

$$I_{C2} = \alpha_2 I + I_{C02} = I_{B1}$$

$\alpha$  → ratio of collected current to injected current.

$I = I_{C1} + I_{C2}$  (According to KCL)

$$I = (\alpha_1 + \alpha_2) I + I_{C01} + I_{C02}$$



$$\Rightarrow I = \frac{I_{C01} + I_{C02}}{1 - (\alpha_1 + \alpha_2)}$$

current  $I$ , through the device is small  $\rightarrow A_s(\alpha_1 + \alpha_2)$   
 $\alpha$  is small compared to unity.



When  $(\alpha_1 + \alpha_2) \rightarrow$  approaches to unity, then this derivation is no longer valid.

Three bias states of p-n-p-n diodes

1) Forward blocking state

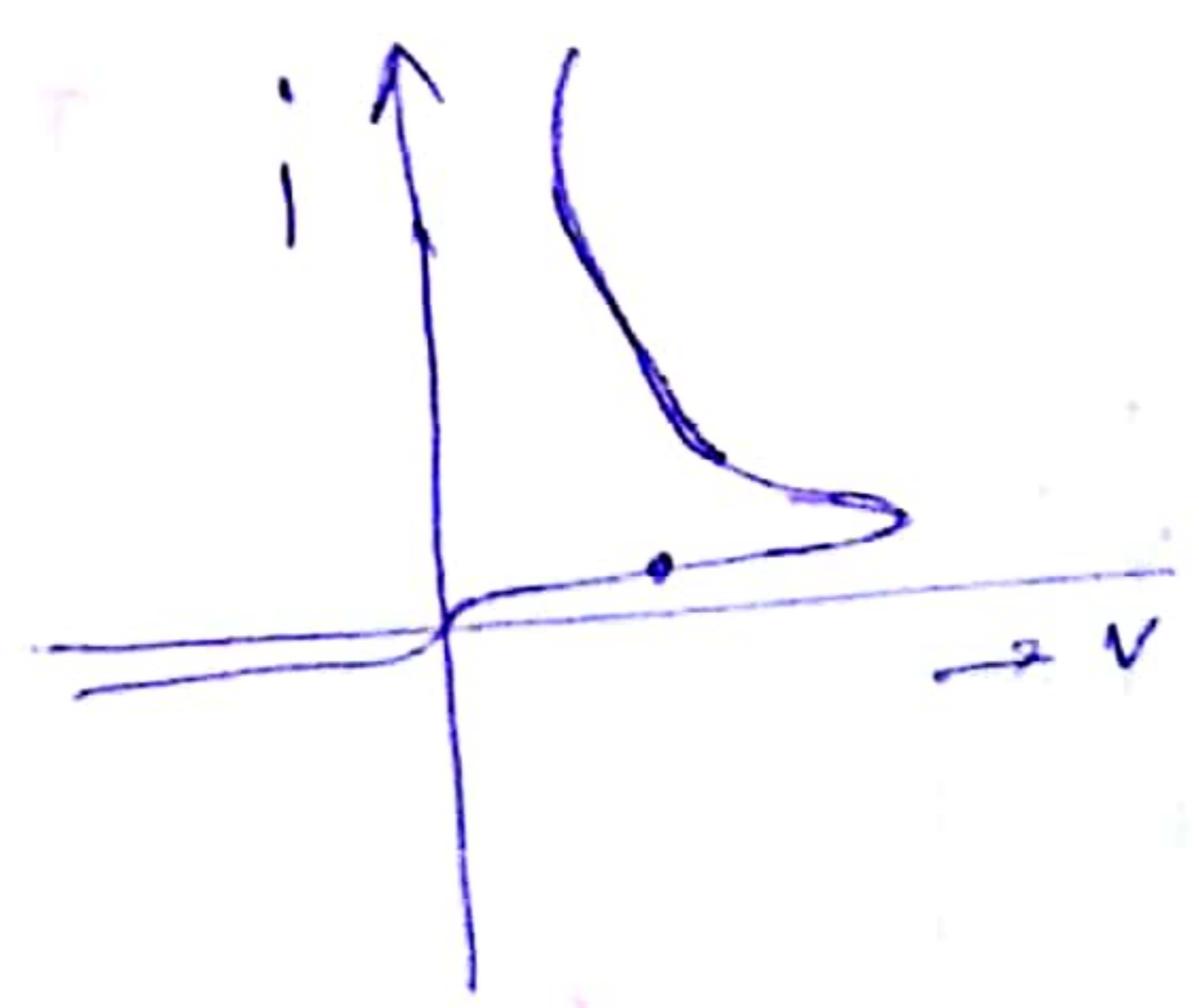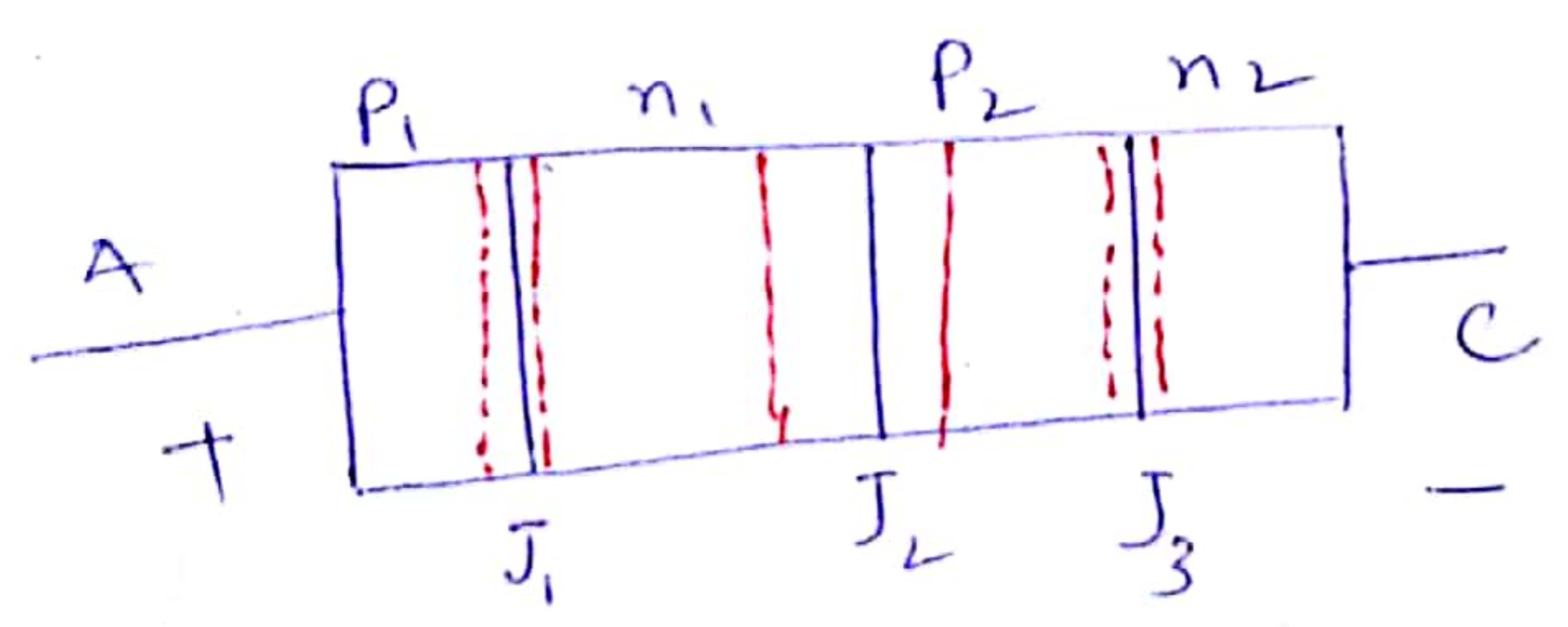

2) Forward-conducting state

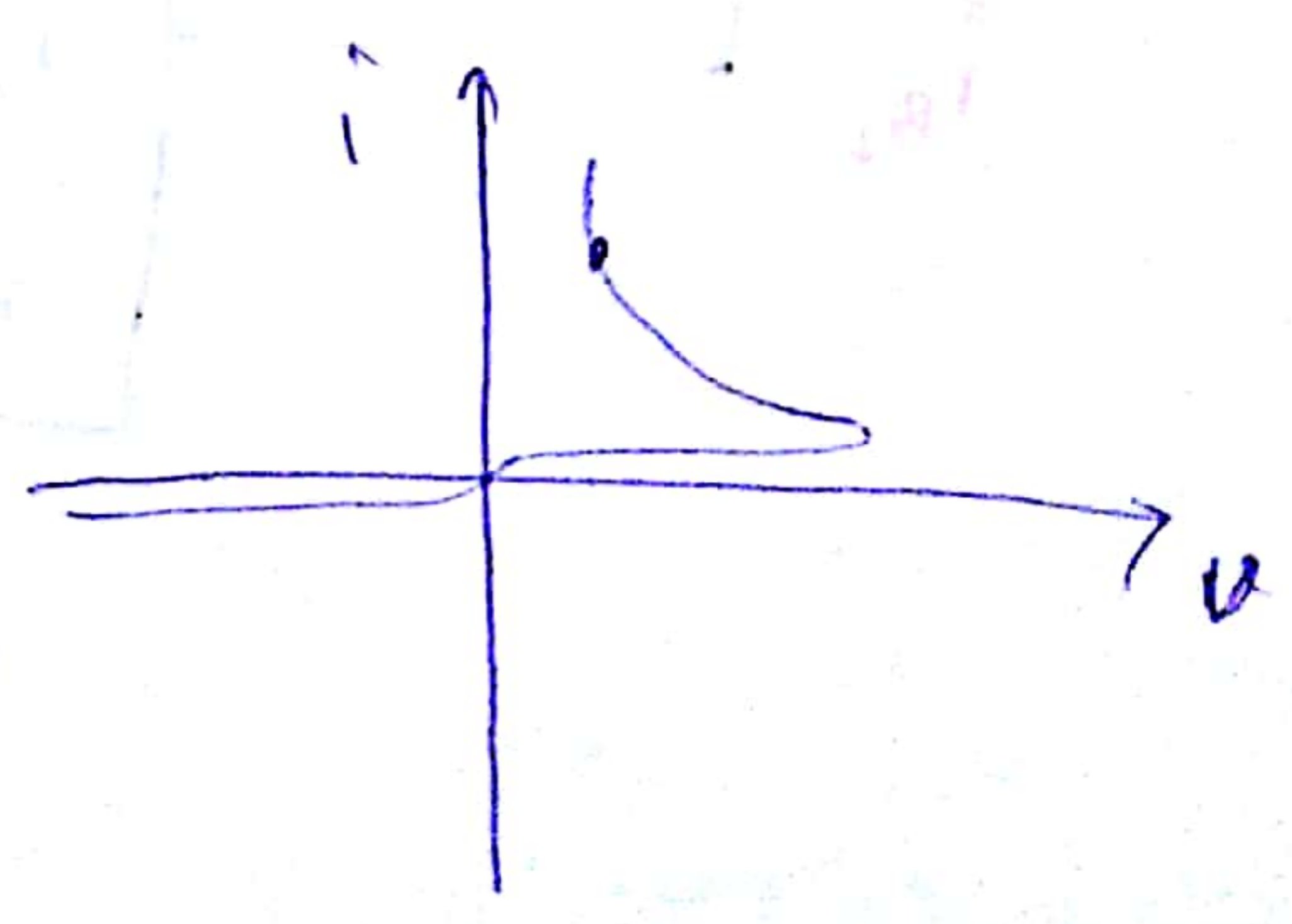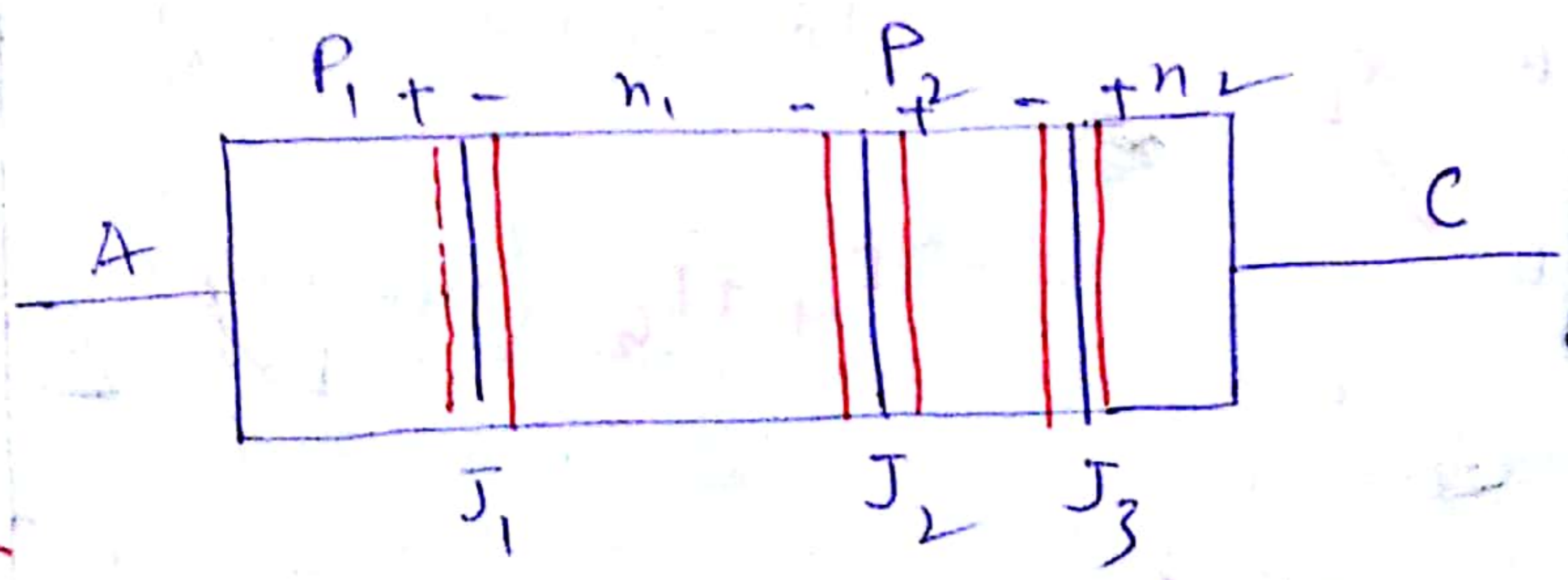

$I = I_s (e^{V/V_T} - 1)$   
 $I_s = A_s q n_i^2 ( \frac{1}{N_A L_p} + \frac{1}{N_D L_n} )$

### 3) Reverse Blocking State

